
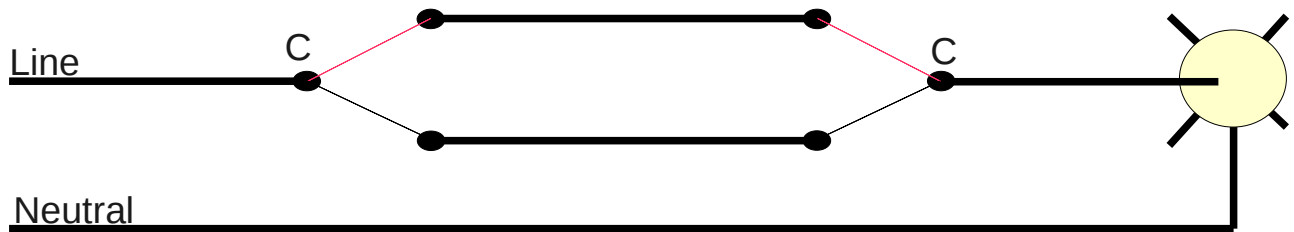


Three Ways to Wire a Three-Way Switch

Common In – Common Out

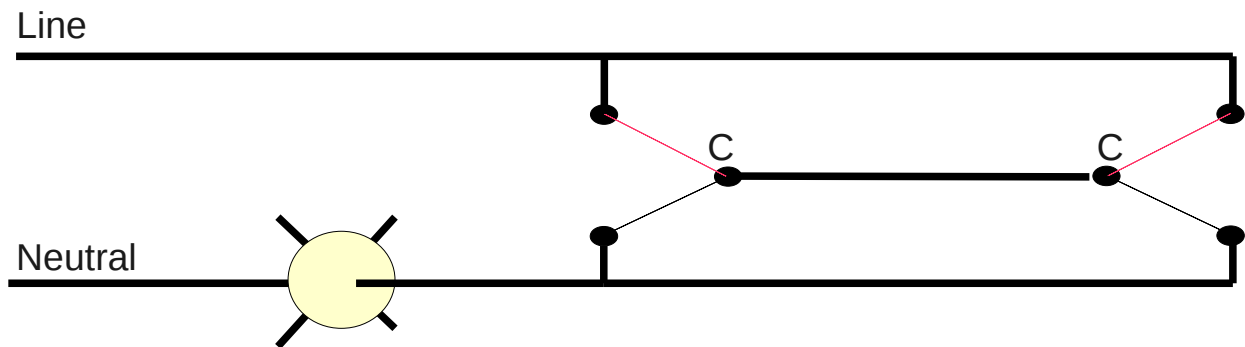

Traveller In – Traveller Out



Illegal

